

Givens

$$Z_o = 50\Omega, \quad f = 9.5GHz$$

$$\text{Copper thickness} = 1 \text{ oz/ft}^2 = 34 \mu m$$

Substrate: Rogers RT/Duroid 5880

$$h = 787.41 \mu m, \quad \epsilon_r = 2.20 \pm 0.04, \quad \tan\delta = 0.0009 @ 10 GHz$$

npn type BJT BFG410W fabricated by NXP semiconductors

$$I_c = 6mA, \quad V_{ce} = 2V$$

S parameters @9.5GHz are Extracted from Spar_BFG410W_commonemitter2V6mA file

$$[S] = \begin{bmatrix} 0.608\angle 34.757^\circ & 0.151\angle -52.987^\circ \\ 1.603\angle -81.484^\circ & 0.238\angle 49.648^\circ \end{bmatrix}$$

Matching Networks Microstrip TL — radial stub and $\lambda/4$ transmission line $\left(\lambda = \lambda_g = \frac{\lambda_o}{\sqrt{\epsilon_{eff}}} \right)$

Specs

- Stability: stable over the entire useful bandwidth of the device
- $G = G_{T,max}$ at the design frequency
- $S_{11}|_{amp}, S_{22}|_{amp}$: minimize
- Only open-circuited shunt stubs should be used
- BW : maximize, based on a narrowband design (The pair of networks that are to be used in the end should be selected such that the bandwidth of the amplifier is maximized)
- Amplifier must be DC-isolated by blocking capacitors
- Layout has space between the launcher microstrip lines and the surface mount capacitors
- Layout must take into consideration the physical dimensions of the transistor, capacitors, and resistors. The capacitors and resistors are surface-mounted ones. You can use the dimensions of the 0603 package for the capacitors and resistors.

Stability

Rollet's condition and μ -stability test

A device will be unconditionally stable if:

- $K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|} > 1$
- $|\Delta| = |S_{11}S_{22} - S_{12}S_{21}| < 1$
- $\mu = \frac{1 - |S_{11}|^2}{|S_{22} - S_{11}^* \Delta| + |S_{21}S_{12}|} > 1$

} Rollet's condition

$$\Delta = 0.366 \angle 59.891^\circ$$

$$|\Delta| = 0.366 < 1$$

$$K = 1.462 > 1$$

The device is unconditionally stable @9.5GHz

Another Solution

$$\mu = 1.849 > 1$$

The device is unconditionally stable @9.5GHz

Gain


Gain equations

- The transducer power gain is:


$$G_T = \frac{P_L}{P_{AVS}} = \frac{(1-|\Gamma_s|^2)}{|1-\Gamma_{in}\Gamma_s|^2} |S_{21}|^2 \frac{(1-|\Gamma_L|^2)}{|1-S_{22}\Gamma_L|^2}$$

$$G_T = \frac{P_L}{P_{AVS}} = \frac{(1-|\Gamma_s|^2)}{|1-s_{11}\Gamma_s|^2} |S_{21}|^2 \frac{(1-|\Gamma_L|^2)}{|1-\Gamma_{out}\Gamma_L|^2}$$

**Maximum gain
amplifier design**

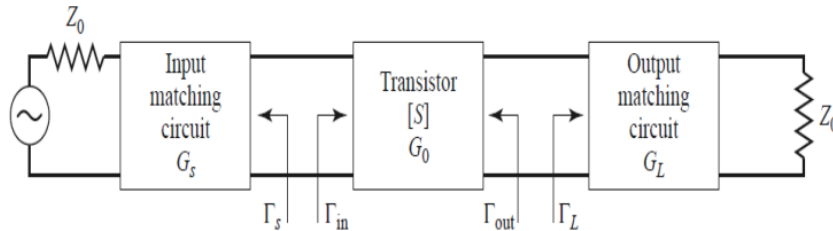

Maximum gain design (conjugate matching)

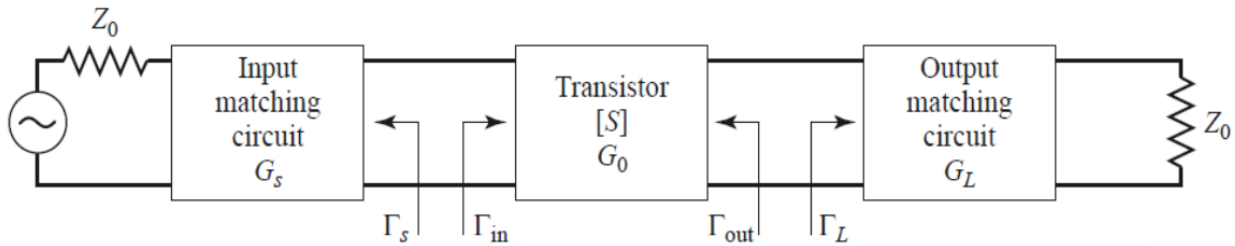

- $\Gamma_{in} = \Gamma_s^*$ and $\Gamma_{out} = \Gamma_L^*$

- $\Gamma_s^* = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1-S_{22}\Gamma_L}$

- $\Gamma_L^* = S_{22} + \frac{S_{12}S_{21}\Gamma_s}{1-S_{11}\Gamma_s}$

- $\Gamma_s = \frac{B_1 \pm \sqrt{B_1^2 - 4|C_1|^2}}{2C_1}$

- $\Gamma_L = \frac{B_2 \pm \sqrt{B_2^2 - 4|C_2|^2}}{2C_2}$

$$G_{Tmax} = G_{smax} G_o G_{Lmax}$$

$$G_{Tmax} = \frac{1}{(1-|\Gamma_s|^2)} |S_{21}|^2 \frac{(1-|\Gamma_L|^2)}{|1-S_{22}\Gamma_L|^2}$$

$$G_{Tmax} = \frac{|S_{21}|}{|S_{12}|} (K - \sqrt{K^2 - 1})$$

$$B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2$$

$$B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2$$

$$C_1 = S_{11} - \Delta S_{22}^*$$

$$C_2 = S_{22} - \Delta S_{11}^*$$

Law4

$$G_{T,max} = 4.199 = 6.231 \text{ dB}$$

Another Solution

$$B_1 = 1.179$$

$$B_2 = 0.553$$

$$C_1 = 0.53\angle 38.669^\circ$$

$$C_2 = 0.099\angle 118.652^\circ$$

$$\Gamma_s = \cancel{1.599\angle -38.669^\circ (rejected)}, \quad 0.625\angle -38.669^\circ$$

$$\Gamma_L = \cancel{5.404\angle -118.652^\circ (rejected)}, \quad 0.185\angle -118.652^\circ$$

$$\Gamma_{in} = 0.625\angle 38.669^\circ$$

$$\Gamma_{out} = 0.185\angle 118.652^\circ$$

Law1

$$G_T = 4.199 = 6.231dB$$

Law2

$$G_T = 4.199 = 6.231dB$$

Law3

$$G_T = 4.199 = 6.231dB$$

Microstrip TL Design


Microstrip transmission lines: $\frac{W}{d}$

For a given characteristic impedance Z_0 and dielectric constant ϵ_r , the W/d ratio can be found as:

$$\circ \frac{W}{d} = \begin{cases} \frac{8e^A}{e^{2A}-2} & \text{for } W/d < 2 \\ \frac{2}{\pi} \left[B - 1 - \ln(2B - 1) + \frac{\epsilon_r - 1}{2\epsilon_r} \left\{ \ln(B - 1) + 0.39 - \frac{0.61}{\epsilon_r} \right\} \right] & \text{for } W/d > 2 \end{cases}$$

$$\circ A = \frac{Z_0}{60} \sqrt{\frac{\epsilon_r + 1}{2}} + \frac{\epsilon_r - 1}{\epsilon_r + 1} \left(0.23 + \frac{0.11}{\epsilon_r} \right)$$
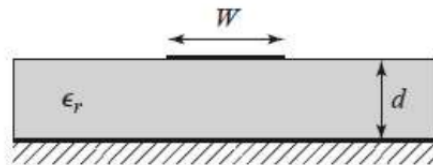
$$\circ B = \frac{377\pi}{2Z_0\sqrt{\epsilon_r}}$$




$$A = 1.159 \rightarrow \frac{W}{d} = 3.126 < 2 \text{ (rejected)}$$

$$B = 7.985 \rightarrow \frac{W}{d} = 3.081 > 2$$

Microstrip transmission lines: ϵ_e

The effective dielectric constant of a microstrip line is given

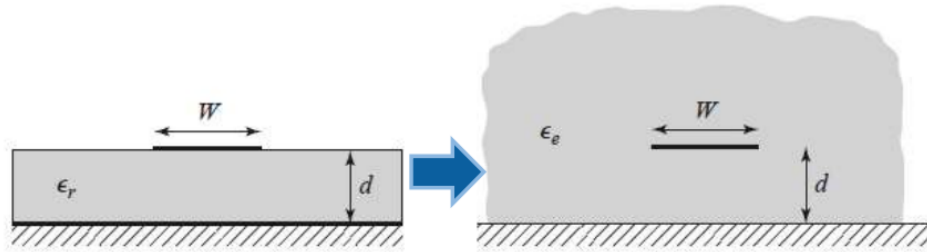approximately by: $\epsilon_e = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \frac{1}{\sqrt{1 + 12d/W}}$.




$$\epsilon_{eff} = 1.871$$

$$\lambda = \lambda_g = \frac{\lambda_o}{\sqrt{\epsilon_{eff}}} = \frac{c_o}{f \sqrt{\epsilon_{eff}}} = 0.023069m$$

$$\lambda = 23.069mm \rightarrow \frac{\lambda}{4} = 5.767mm$$

Input and Output Matching Network

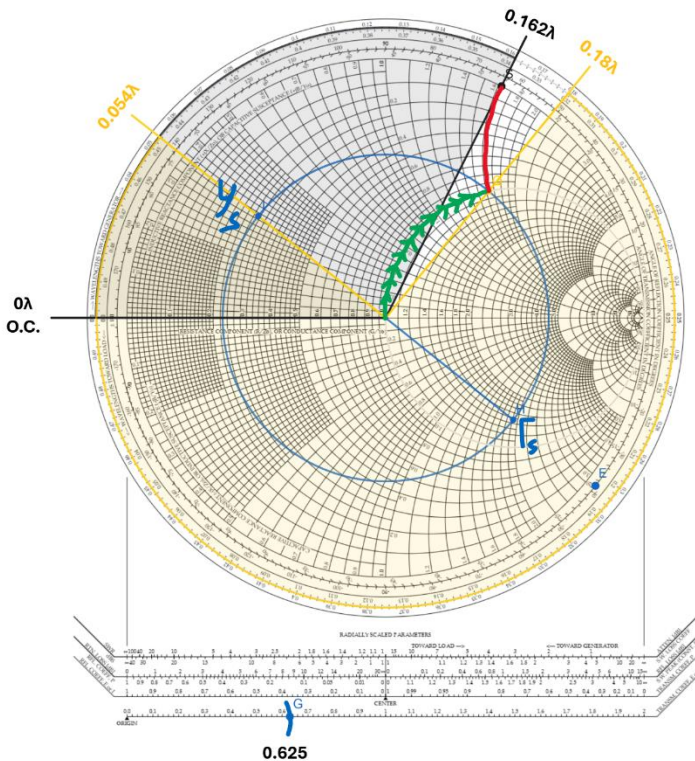

Solution1

$$l = 0.162\lambda - 0\lambda$$

$$l = 0.162\lambda + \frac{m\lambda}{2}, m = 0, 1, 2, \dots$$

$$l = 0.162\lambda = 58.32^\circ$$

$$l = 3.737mm$$

$$d = 0.054\lambda - 0.18\lambda$$


$$d = -0.126\lambda$$

$$d = -0.126\lambda + 0.5\lambda$$

$$d = 0.374\lambda + \frac{m\lambda}{2}, m = 0, 1, 2, \dots$$

$$d = 0.374\lambda = 134.64^\circ$$

$$d = 8.628mm$$

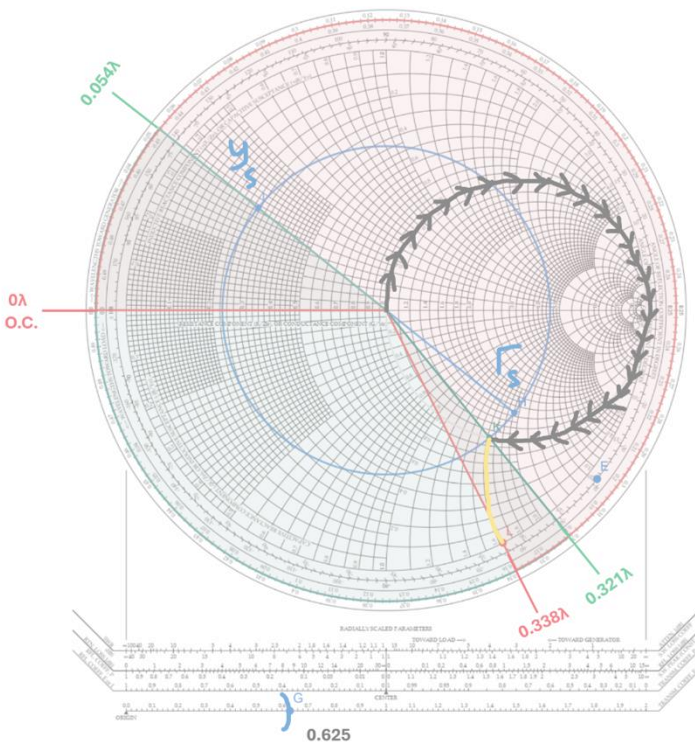

Solution2

$$l = 0.338\lambda - 0\lambda$$

$$l = 0.338\lambda + \frac{m\lambda}{2}, m = 0, 1, 2, \dots$$

$$l = 0.338\lambda = 121.68^\circ$$

$$l = 7.797mm$$

$$d = 0.054\lambda - 0.321\lambda$$

$$d = -0.267\lambda$$


$$d = -0.267\lambda + 0.5\lambda$$

$$d = 0.233\lambda$$

$$d = 0.233\lambda + \frac{m\lambda}{2}, m = 0, 1, 2, \dots$$

$$d = 0.233\lambda = 83.88^\circ$$

$$d = 5.375mm$$

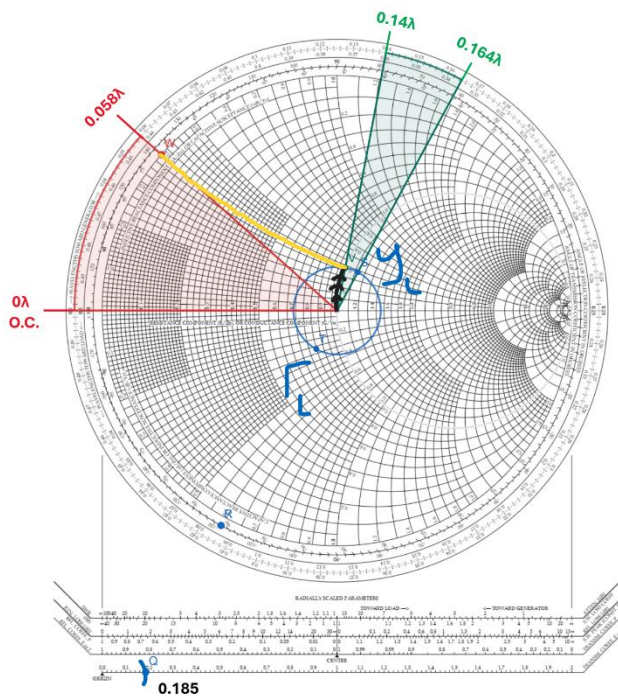

Solution1

$$l = 0.058\lambda - 0\lambda$$

$$l = 0.058\lambda + \frac{m\lambda}{2}, m = 0, 1, 2, \dots$$

$$l = 0.058\lambda = 20.88^\circ$$


$$l = 1.338\text{mm}$$

$$d = 0.164\lambda - 0.14\lambda$$

$$d = 0.024\lambda + \frac{m\lambda}{2}, m = 0, 1, 2, \dots$$

$$d = 0.024\lambda = 8.64^\circ$$

$$d = 0.554\text{mm}$$

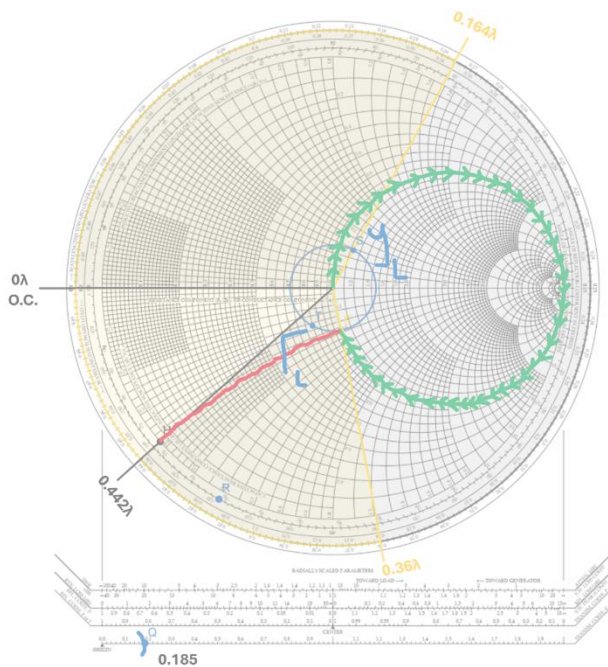

Solution2

$$l = 0.442\lambda - 0\lambda$$

$$l = 0.442\lambda + \frac{m\lambda}{2}, m = 0, 1, 2, \dots$$

$$l = 0.442\lambda = 159.12^\circ$$

$$l = 10.197\text{mm}$$

$$d = 0.164\lambda - 0.36\lambda$$

$$d = -0.196\lambda$$


$$d = -0.196\lambda + 0.5\lambda$$

$$d = 0.304\lambda + \frac{m\lambda}{2}, m = 0, 1, 2, \dots$$

$$d = 0.304\lambda = 109.44^\circ$$

$$d = 7.013\text{mm}$$

Input Matching Network

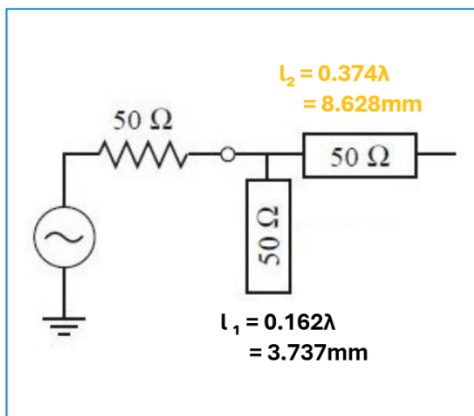

Output Matching Network

